





## INDEX

Sl.No.	Date	DESCRIPTION	Page No.	Marks	Signature
1	20/11/23	Program on Structural	1-2	8	<del>JF</del>
2	4/12/23	Program on half adder and full adder and Subtractor	3-6	10	<del>JF</del>
3	18/12/23	Program on multiplex	7-9	10	<del>JF</del>
4	18/1/24	Program On de-multiplex	10-12	10	<del>JF</del>
5	1/1/24	Program on flip flop	13-15	10	<del>JF</del>
6	22/1/24	program on 4 bit full adder	16-17	10	<del>JF</del>
7	12/2/24	Program on BCD adder	17-18	16	<del>JF</del>
8	12/2/24	Program On behavioural model	19-20	10	<del>JF</del>

Truth table

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1

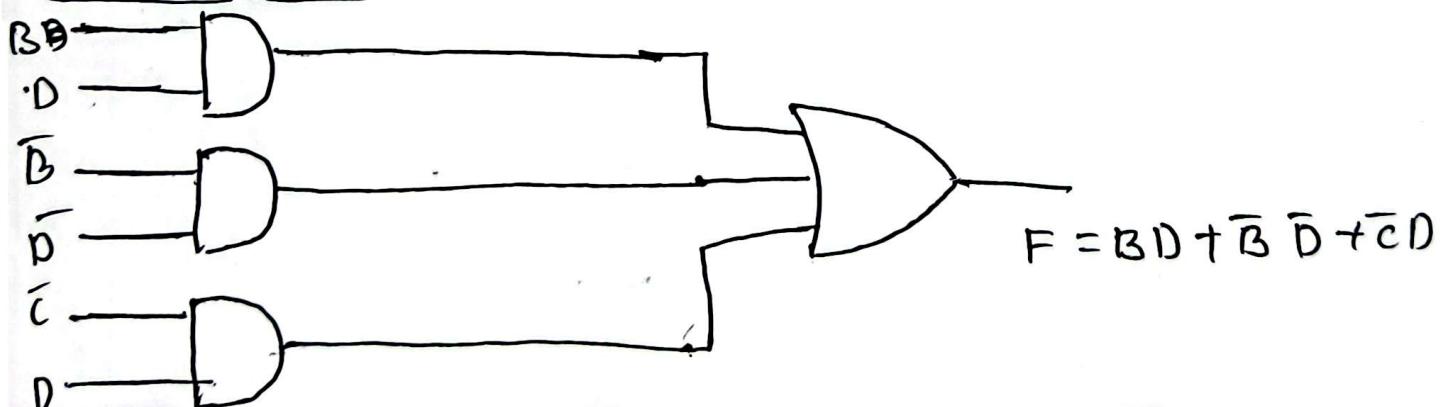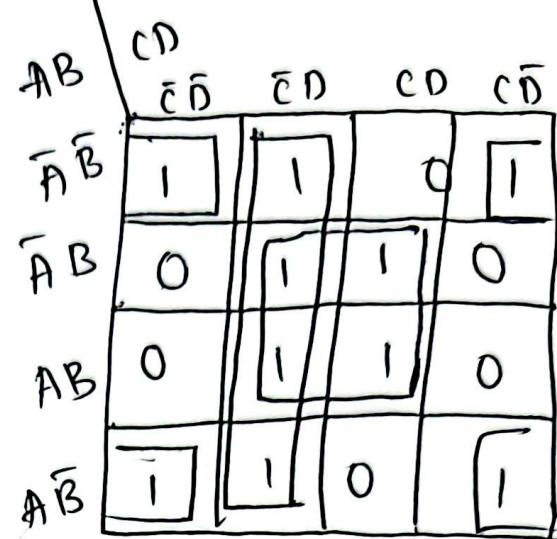Logic gateK-map



TITLE

Given a 4 variable logic expression. Simplify it using appropriate technique & stimulate the same using basic gate  $F(A, B, C, D) = \sum m(0, 1, 2, 5, 7, 8, 9, 10, 13, 15)$   
Aim:- To Simplify the given 4-variable logic expression using K-map & Stimulate using basic gates

Theory :- A K-map is a graphical representation of truth-table which is a systematic way to simplify & optimize boolean algebra expression used in digital circuit design. K-maps are helpful for minimizing the no of logic gates in a given logic func

Basic Concepts :-

Truth Table :- A truth-table is a tabular representation of all possible input combination & their corresponding output values for a logic func. It helps define the behaviour of the func.

Boolean :- A mathematical func System used to manipulate binary Variable & perform logical operation such as AND, OR & NOT. It is essential for Simplify & optimizing logic func



TITLE

Program :

module. AOI - structural (A,B,C,D,F);  
input A,B,C,D;  
output F;  
assign F =  $\neg(C \cdot (A \oplus B)) \mid (C \oplus D)$ ;  
endmodule

Program

module. AOI - structural (F,A,B,C,D);  
input A,B,C,D;  
output F;  
assign F =  $(B \oplus D) \mid (\neg C \oplus D)$ ;  
end module;

The image shows a software application window with a dark-themed interface. On the left, there is a sidebar containing five entries, each with a blue circular icon and text: 'IAOL\_structural/F', 'IAOL\_structural/A', 'IAOL\_structural/H', 'IAOL\_structural/C' (which is highlighted in white), and 'IAOL\_structural/D'. To the right of the sidebar is a vertical column of file names: 'S1', 'S20', 'S20', 'S1', and 'S20'. Below this column is a large, empty grid area consisting of 12 columns and 10 rows, with a yellow vertical line running through the 6th column.

IAOL_structural/F	S1										
IAOL_structural/A	S20										
IAOL_structural/H	S20										
IAOL_structural/C	S1										
IAOL_structural/D	S20										


## Truth table for half adder

n	A	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$S = A \oplus B$$

$$C = AB$$

## Logic gate for half adder

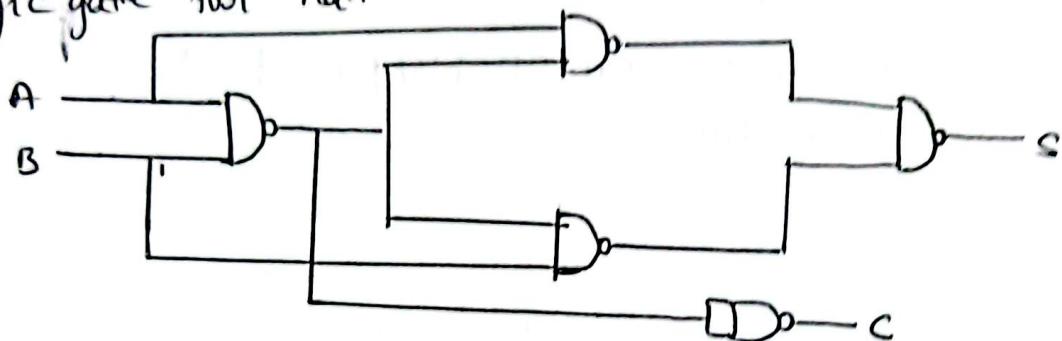


## Truth table for full adder

A	B	C <sub>in</sub>	S	C
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$S = A \oplus B \oplus C$$

$$C_{in} = AB + BC_{in} + AC_{in}$$

## Logic gate for full adder

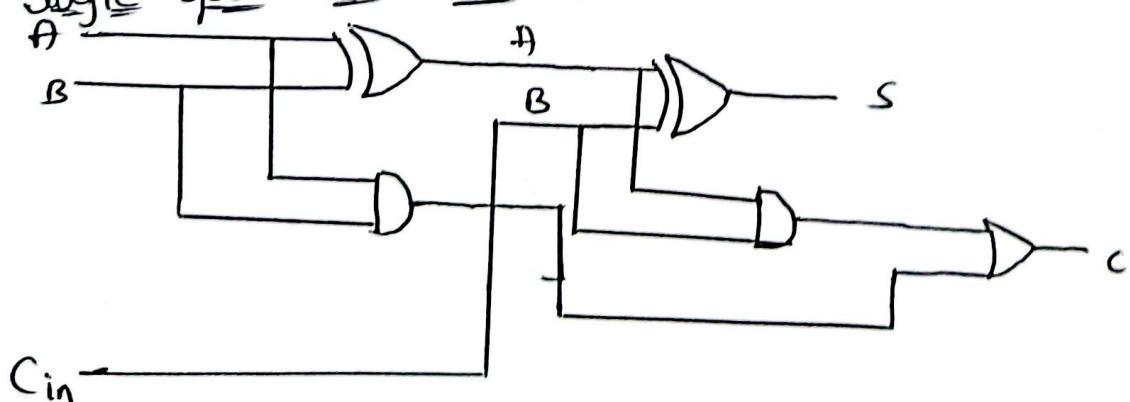



TITLE

Design Verilog HDL to implement Binary Address-Subtractors Half & full adder, Half & full-subtractor

Aims- To design & verify

i) Half adder & full adder

ii) Half subtractor & full subtractor

Theory:-

Half adder: A Combinational logical circuit that perform the addition of 2 bits of data. A & B is called one of which is Sum bit & and the other is the carry bit C. The boolean func are

$$S = A \oplus B \quad C = AB$$

Full Adder: A Combinational logical circuit that perform the half adder which doesn't take carry bit from its previous stage into the carry bit in previous stage. Called Carry-in-bit that adds 2-bits, A & B. & carry a in Cin, Cin is called a full Adder. The boolean func are.

$$S = x \oplus y \oplus \text{Cin} \quad C = xy + \text{Cin}(x \oplus y)$$



TITLE

Half Subtraction :- Subtracting a single bit binary value B another A produces a difference bit P & a below out bit B-out. The operation is called half subtractor & the circuit to realize it is called half-subtractor. The boolean func are

$$S = A \oplus B C = A' B$$

Full Subtraction :- Subtracting a single bit binary value B, (in func) a single bit value. It produces a difference bit D & a boolean Out B bit this is called full subtraction. The boolean func are

$$D = (x \oplus y) \oplus \text{cin} \quad B = A' B + A' (\text{cin}) + B (\text{cin})$$


## Half Subtractor Truth Table

A	B	D	$B_1$
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

$$D = A \oplus B$$

$$B_1 = \bar{A}B$$

## Logic gate Half Subtractor

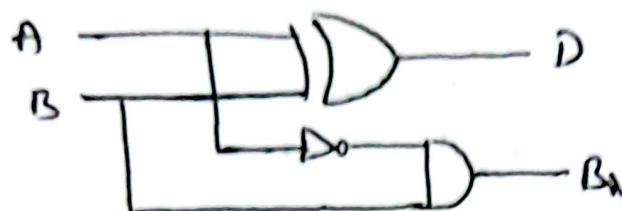


## Full Subtractor - Truth Table

A	B	$C_{in}$	D	$B_1$
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

$$D = A \oplus B \oplus C$$

$$B_1 = \bar{A}B + B C_{in} + \bar{A} C_{in}$$

## Logic gate - full subtractor

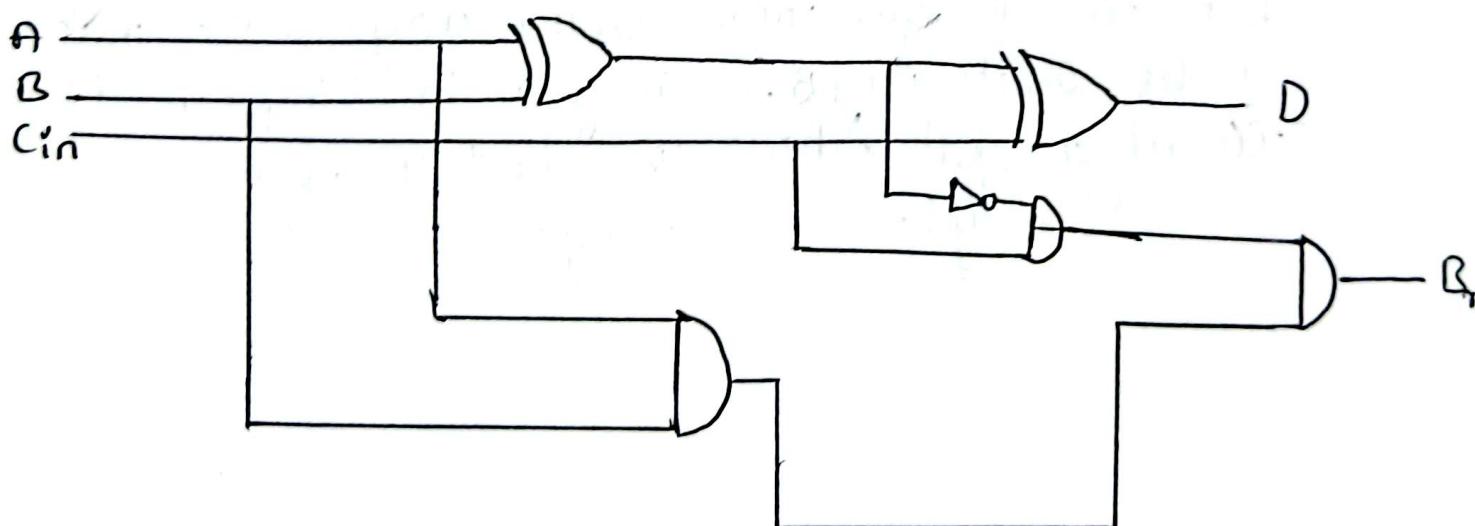





TITLE

Program on half Adder  
module half-adder(a,b,sum,carry);  
input a,b;  
output sum, carry;  
assign sum = a^b;  
assign carry = (a&b);  
endmodule;

Program on Full adder  
module full-adder(a,b,c,sum,carry);  
input a,b,c;  
Output sum = a^b^c;  
assign sum = (a&b)|(a&c)|(c&b);  
endmodule.

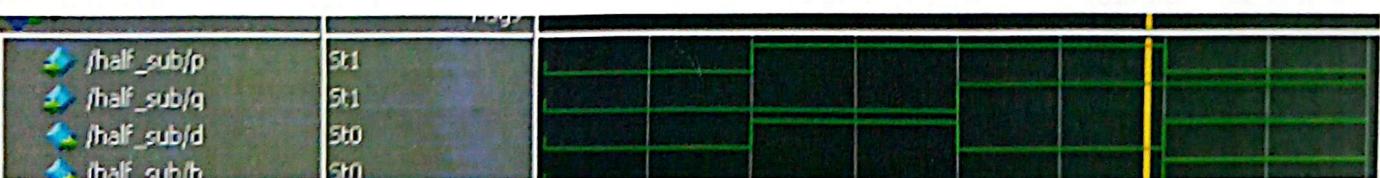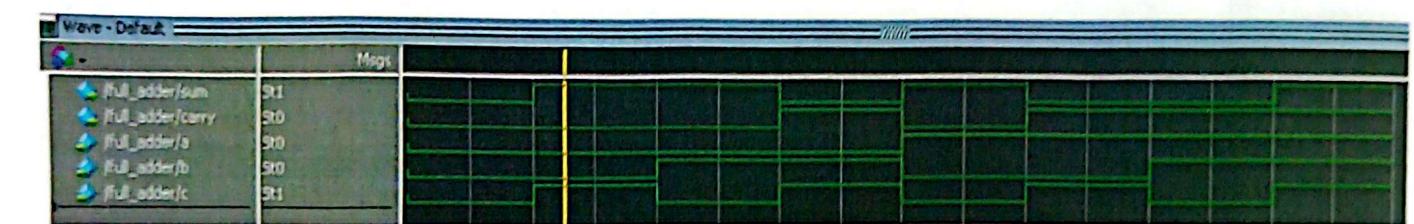Program on half Subtractor  
module half-subtractor(A,B,D,B1);  
input A,B ;  
Output D, B1 ;  
assign D = A^B ;  
assign B1 = (~A)&B ;  
endmodule





TITLE

Program on full Subtractor  
module full-Subtractor ( $A, B, Cin, D, B_i$ );  
input  $A, B, Cin$ ;  
output  $D, B_i$ ;  
assign  $D = A' B' Cin$ ;  
assign  $B_i = (n(A \oplus B)) \mid (n(A' B') \& Cin)$ ;  
end module





TITLE

Design Verilog program to implement different types of multiplex 2:1, 4:1, 8:1

Aim :- Implement different types of multiplex 2:1, 4:1  
8:1


Theory :-

- 2:1 multiplex :- It has two input & one select line
- 4:1 multiplex :- It has 4 input & 2 select lines
- 8:1 multiplex :- It has 8 input & 3 select lines

A multiplex is a combination circuit that selects binary information from many input lines & direct it to a single output line. The selection of particular input lines is controlled by a set of selection lines.


Truth table of 2:1 multiplexer

Sel.	Y
0	$i_0$
1	$i_1$

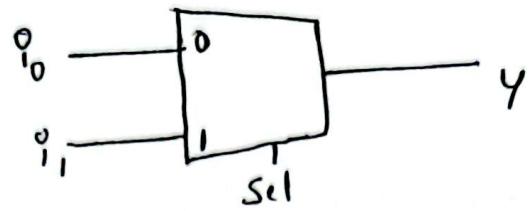

Truth table 4:1 multiplexer block diagram


Sel[0]	Sel[1]	Y
0	0	$i_0$
0	1	$i_1$
1	0	$i_2$
1	1	$i_3$

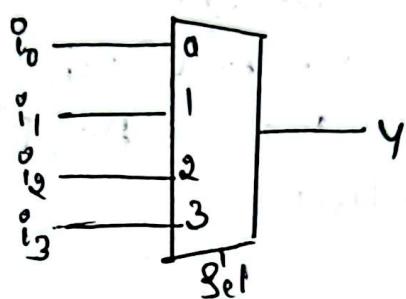

block diagram

Truth table 8:1 Multiplexer

S <sub>3</sub>	S <sub>2</sub>	S <sub>1</sub>	S <sub>0</sub>	Y
0	0	0	$i_0$	
0	0	1	$i_1$	
0	1	0	$i_2$	
0	1	1	$i_3$	
1	0	0	$i_4$	
1	0	1	$i_5$	
1	1	0	$i_6$	
1	1	1	$i_7$	

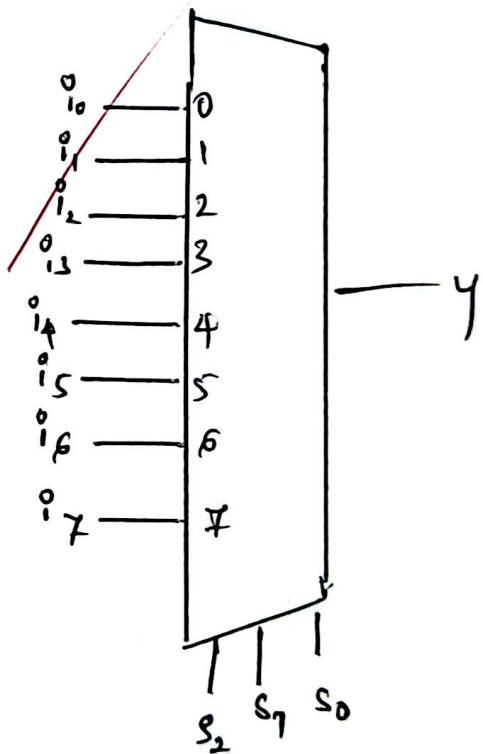



TITLE

Program On 2:1 multiplex  
module m21(D0, D1, S, Y);  
input wire D0, D1, S;  
output reg Y;  
always @ (D0 or D1 or S)  
begin  
if (S)  
Y = D1;  
else  
Y = D0;  
end  
endmodule

Program On 4:1 multiplex  
module mux4(in, sel, out);  
input [3:0] in;  
input [1:0] sel;  
output reg out;  
always @ (sel)  
begin  
case (sel)  
0' b00: out = in[0];  
0' b01: out = in[1];  
0' b10: out = in[2];  
0' b11: out = in[3];  
end case  
end  
endmodule

	Msgs
/mux2x1/0	\$t0
/mux2x1/1	\$t1
/mux2x1/S	\$t0
/mux2x1/Y	0

Diagram illustrating the output of the 2x1 MUX. The output is connected to the input of a 4x1 MUX.

	Msgs
/mux41/in	0000
[3]	\$t0
[2]	\$t0
[1]	\$t0
[0]	\$t0
/mux41sel	00
[1]	\$t0
[0]	\$t0
/mux41/out	0



ANJUMAN INSTITUTE OF TECHNOLOGY  
& MANAGEMENT  
ANJUMANABAD, BHATKAL - 581 320

PAGE NO. : ..... 09 .....  
DATE : ..... .....  
EXP. NO. : ..... 03 .....

TITLE

Program On 8:1 multiplex  
module mux81(y,a,s)

input [7:0] a;

input [2:0] s;

output reg y;

always @ (a,s)

begin

case (s)

3' b000: y = a[0];

3' b001: y = a[1];

3' b010: y = a[2];

3' b011: y = a[3];

3' b100: y = a[4];

3' b101: y = a[5];

3' b110: y = a[6];

3' b111: y = a[7];

end case

end

end module



TITLE

Design Verilog program to implement types of De-multiplex

Aim & Program On De-multiplex

Theory :-

A demultiplexer is a Combinational Circuit that works exactly opposite to a multiplexer. A Demux has a single input line that connects to any one of the output lines based on its control input signal or selection lines.

There are 2 types of Demultiplexer


1:2 Demultiplexer : It has one select line and 2 output lines

1:4 Demultiplexer : It has one Select line & 4 output lines

Truth table 1:2 DEMUX

Sel	$y_0$	$y_1$
0	1	0
1	0	1


Block Diagram

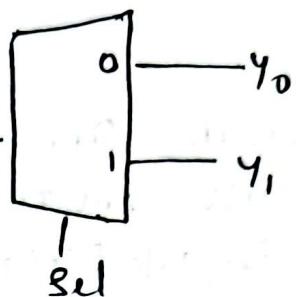

Truth table 1:4 DEMUX

sel [0]	sel [1]	$y_0$	$y_1$	$y_2$	$y_3$
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

Block Diagram

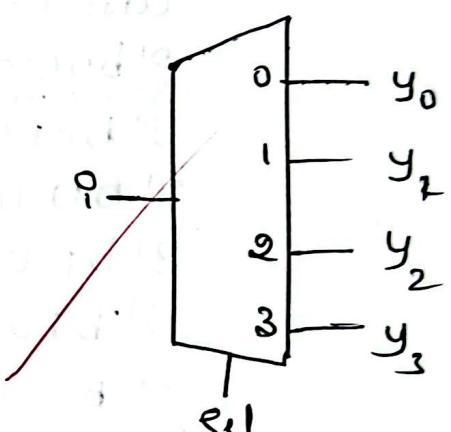

Truth table 1 to 4 DEMUX

input		out put				
$s_1$	$s_2$	a-in	$y_3$	$y_2$	$y_1$	$y_0$
0	0	1	0	0	0	1
0	1	1	0	0	1	0
1	0	1	0	1	0	0
1	1	1	1	0	0	0



ANJUMAN INSTITUTE OF TECHNOLOGY  
& MANAGEMENT  
ANJUMANABAD, BHATKAL - 581 320

PAGE NO. : ..... 11 .....

DATE : .....

EXP. NO. : ..... 04 .....

TITLE

Program On demux

module demux1\_4(a-in, sel, y);

input a-in;

input [1:0]sel;

output [3:0] y;

begin

case(sel)

2'b00 = begin y[0]=a-in;

y[1]= 1'b0;

y[2]= 1'b0;

y[3]= 1'b0;

end

2'b01= begin y[0]=1'b0;

y[1]= a-in;

y[2]= 1'b0;

y[3]= 1'b0;

end

2'b10: begin y[0]=1'b0;

y[1]= 1'b0;

y[2]= a-in;

y[3]= 1'b0;

end

Timing diagram showing the output of a 4-to-1 multiplexer (Demux1\_4) based on the selection input (sel).

The sel input has four states: 00, 01, 10, and 11. The corresponding outputs are 0001, 0010, 0100, and 1000 respectively.

	00	01	10	11
0001	1	0	0	0
0010	0	1	0	0
0100	0	0	1	0
1000	0	0	0	1



TITLE

$2^{'b}11 : begin \quad y[0] = 'b0;$

$y[1] = 'b0;$

$y[2] = 'b0;$

$y[3] = a - in;$

end

default :  $y = 3^{'b}000;$

endcase

end

endmodule.



TITLE

Design Verilog program for implementation of various types of flip-flops such as SR, JK and D

Aim :-

To design and implement various types of flip-flop like D using Verilog HDL

Verilog code for JK flip-flop  
module jk\_ff(jk, q, qb)

input [1:0] jk;

input clk;

output q;

output qb;

always @ (posedge clk)

begin

case (jk)

2'b00: q=q;

2'b01: q=0;

2'b10: q=1;


2'b11: q=~q;

endcase

end

endmodule

## JK FLIPFLOP

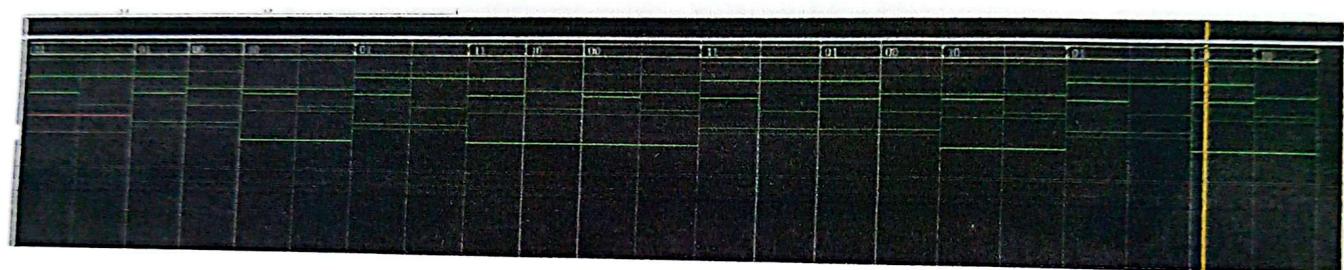



**ANJUMAN INSTITUTE OF TECHNOLOGY  
& MANAGEMENT**  
ANJUMANABAD, BHATKAL - 581 320

PAGE NO. : 14  
DATE : .....  
EXP. NO. : 05

TITLE

Verilog Code for SR-flipflop  
module SR-ff(sr,clk,q,qb);  
input [1:0]sr;  
input Eclk;  
output q,qb;  
reg q,qb;  
always @ (posedge clk)  
begin  
case(sr)  
2'b00: q=q;  
2'b01: q=0;  
2'b10: q=1;  
2'b11: q = 1'bz;  
endcase  
end  
endmodule



SR FLIPFLOP





ANJUMAN INSTITUTE OF TECHNOLOGY  
& MANAGEMENT  
ANJUMANABAD, BHATKAL - 581 320

PAGE NO. .... 15 .....

DATE : .....

EXP. NO. .... 05 .....

TITLE

Verilog code for D-flip flop  
module clff(d,clk,a,q,b)

input d;

input clk;

output q,qb;

reg q,qb;

always@ (posedge clk)

begin .

case (d)

1'b0: q=0;


1'b1: q=1;

endcase

qb=q;

end

endmodule

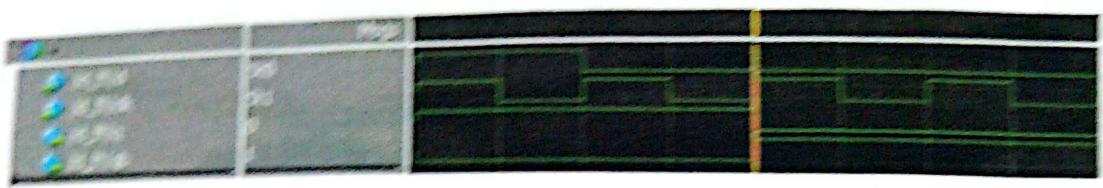



TITLE

Design a ~~half~~ 1 bit full adder and Subtract  
or and stimulate the same using basic gates

Aim :- To design 4 bit full adder using logic  
gates

VHDL code for 1-bit full adder

```
module rippleverilog (sum, cout, a, b, cin);
    input a, b, cin;
    output sum, cout;
    wire s1, c1, s2;
    xor (s1, a, b);
    xor (sum, s1, cin);
    and (c1, a, b);
    and (c2, s1, cin);
    or (cout, c1, c2);
endmodule
```

// origin 4 bit ripple adder

```
module fourbitadder (sum, cout, a, b, cin);
    input [3:0] a;
    input [3:0] b;
    input cin;
    output [3:0] sum;
    output cout;
    wire c1, c2, c3;
    uippleverilog u1 (sum[0], c1, a[0], b[0], cin);
    uippleverilog u2 (sum[1], c2, a[1], b[1], c1);
    uippleverilog u3 (sum[2], c3, a[2], b[2], c2);
    uippleverilog u4 (sum[3], cout, a[3], b[3], c3);
endmodule
```

Fourbitadder

	0000	0010	0011	0100	0101	0110	0111	1000	1001	1010
0000	0001	0010	0011	0100	0101	0110	0111	1000	1001	1010
0010	0001	0010	0011	0100	0101	0110	0111	1000	1001	1010
0011	0001	0010	0011	0100	0101	0110	0111	1000	1001	1010
0100	0010	0100	0110	1000	1010	1100	1110	0000	0010	0100
0101	0010	0100	0110	1000	1010	1100	1110	0000	0010	0100
0110	0010	0100	0110	1000	1010	1100	1110	0000	0010	0100
0111	0010	0100	0110	1000	1010	1100	1110	0000	0010	0100
1000	0100	1000	1010	0000	0010	0100	0110	1000	1001	1010
1001	0100	1000	1010	0000	0010	0100	0110	1000	1001	1010
1010	0100	1000	1010	0000	0010	0100	0110	1000	1001	1010



ANJUMAN INSTITUTE OF TECHNOLOGY  
& MANAGEMENT  
ANJUMANABAD, BHATKAL - 581 320

PAGE NO. : ..... 17 .....

DATE : .....

EXP. NO. : ..... 06 .....

TITLE

~~Uipple verilog r3 [ sum[2], c3, a[1], b2, c2];  
Uipple Verilog r4 [Sum [3], cout ,a[3], b[3], c3);  
endmodule~~

Simulated output of ripple counter is obtained  
step wise of the count incrementing by 1000.

Output of ripple counter is applied to the  
display module.

Output of display module is displayed.

	Mos								
rippleverlog/a	S10								
rippleverlog/b	S11								
rippleverlog/cn	S10								
rippleverlog/sum	S11								
rippleverlog/out	S10								
rippleverlog/s1	S11								
rippleverlog/c1	S10								
rippleverlog/c2	S10								

(0), (1), (2), (3), (4)  
(5), (6), (7), (8), (9)  
and (A), (B), (C), (D)  
etc. are displayed on  
display module.

Output of display module is  
fed back to the feedback station  
which is connected to the  
input of the display module.  
This forms a feedback loop.

Simultaneously, the output of the  
display module is fed to the

display driver module.

Display driver module displays the  
output of the display module.



TITLE

Design Verilog HDL to implement Decimal Adder

Aim:

To design a decimal or BCD adder using Verilog HDL

Verilog code for BCD adder:

```
module bcd_adder(a,b,carry-in,sum,carry);
    input [3:0]a,b;
    input carry_in;
    output [3:0] sum;
    output carry;
    reg [4:0] sum_temp;
    reg [3:0] sum;
    reg carry;
    always @ (a,k,carry_in);
begin
```

Sum-temp = a+b+carry\_in;

If (sum-temp > 9) begin

sum-temp = sum-temp + 6;

carry = 1;

sum = sum-temp [1:0]; end

else begin

carry = 0;

sum = sum-temp[3:0]; end

end

	Mys	0000	0110	0011	0100	1001	1001
/bcd_adder/a	1000	0000	1001	0011	0101	1001	1001
/bcd_adder/b	0010	0000	1001	0011	0101	1001	1001
/bcd_adder/carry_in	St1				1001	1000	1001
/bcd_adder/sum	0001	0000	0110		1001	1000	11001
/bcd_adder/carry	1				01001	10001	
/bcd_adder/sum_temp	10001	00000	10110	00110	01001	10001	



TITLE

Design Verilog HDL to implement Simple Circuit using structured, Data flow an behavioural model

Aim :- To design a Simple Circuit using Standard Structural, data flow and behavioural model

Verilog Code for Structural model

```
module rippleverilog (Sum, Cout, a, b, cin);
    input a, b, cin;
    output Sum, Cout;
    wire s1, c1, c2;
    xor (s1, a, b);
    xor (Sum, s1, cin);
    and (c1, a, b);
    and ((c2, s1, cin));
    or (cout, c1, c2);
endmodule
```

Verilog Code for dataflow model :-

```
module and2( x1, x2, z1);
    output x1, x2;
    output z1;
    wire x1, x2;
    wire z1;
    assign z1 = x1 & x2;
endmodule
```


## Behavioural model

1	2	3	1009	10010	10011	10012	10099	100100	100101	100102	100302	




TITLE

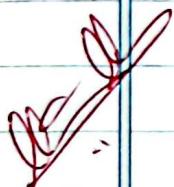Verilog Code for behavioural model  
module mux2x1(input I0,I1,s,output reg Y);  
always @ (c+)  
begin  
if (s)  
Y = I1;  
else  
Y = I0;  
end  
endmodule



### Dataflow model

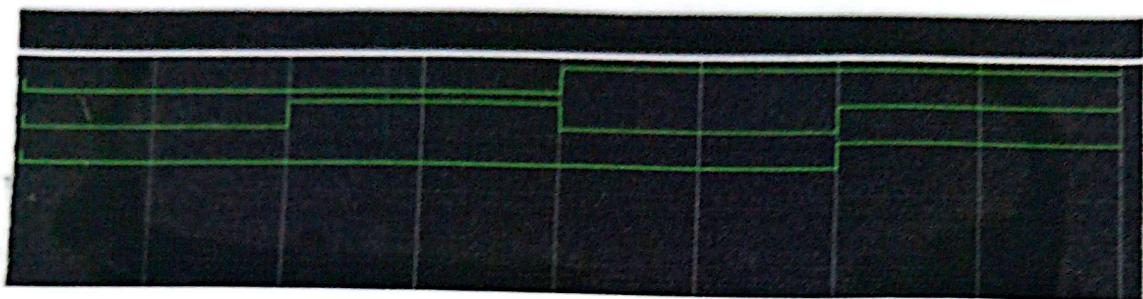

• Dataflow model  
• Data flow graph  
• Directed acyclic graph  
• Parallel execution  
• Pipelining  
• Pipeline factors  
• Pipeline length  
• Pipeline width  
• Pipeline latency  
• Pipeline efficiency  
• Pipeline overhead  
• Pipeline cost  
• Pipeline complexity  
• Pipeline performance

• Pipeline width = number of parallel stages

• Pipeline length

• Pipeline latency = sum of pipeline stages + number of stages - 1